

Q1) a- What is the meaning of single ended signal, differential signal and give example.

b- What is sample and what is hold and when we use them.

[6 pts]

2.39

Q2) Using Temperature sensor (RTD-PT100), in the range (30C to 90C) and using Wheatstone bridge ($V_s=9V$, $R_1=110$, $R_2=120$), and using voltage to frequency converter VFC (scale factor = $10\text{KHz}/1.12V$).

a- Calculate the sensor output range, Wheatstone bridge output range and VFC output range.

b- Using a counter to convert to digital with sampling rate 180 sample/Sec, What is the output range of the counter, what is the value of the output of the counter if the temperature is ~~100C~~ 55°C .

c- Draw Block diagram of the circuit.

[16 pts]

Q3) An accelerometer sensor sensitivity is 0.145mA/g , used for measuring pressure in the range ($\pm 20\text{ g}$). and the value of its output @ 0 g is 5.2mA , using $190\ \Omega$ converting to volt resistance, Design signal condition circuits for bipolar (8 bit) ADC with voltage reference $\pm 4V$.

a) Calculate sensor output range (current, voltage, Binary).

$$= \frac{I_{\text{input}} + V_{\text{ref}}}{R_V}$$

b) What is the digital output of ADC at the acceleration is 8 g .

c) What is the value of acceleration when the digital output is $0DH, 92H$.

[15 pts]

d) If the frequency of the signal is 120Hz and there is unwanted noise with frequency 15KHz , design filter that attenuate the noise to 18% of its value, calculate the effect on the sensor output range.

[05 pts]

Q4) Using RTD with the following table using Quadratic approximation of resistance versus temperature find the value of the RTD at 12.4°C .

Temperature ($^\circ\text{C}$)	0	5	10	15	20
Resistance (Ω)	102.6	105.1	106.3	107.1	108.3

190

103.6

105.1

106.3

107.1

108.3

[08 pts]



Good Luck (Zeyad)

Q(2) RTD-PT 100 , (30°~90° c), wheatstone bridge ($V_s=9V$, $R_1=110\Omega$, $R_2=120\Omega$)
VFC (10 KHZ / 1.12V)

$$\left((30 \times 0.39) + 100 \sim (90 \times 0.39 \frac{\Omega}{^\circ}) + 100 \right) \Rightarrow (111.7 \Omega \sim 135.1) \text{ Sensor o/p}$$

$$R_1 R_4 = R_2 R_3 \Rightarrow 110 * 111.7 = 120 * R_3 \Rightarrow R_3 = 102.39$$

$$V_a = 9 \times \frac{102.39}{102.39 + 110} = 4.339 V, V_{b1} = 9 \times \frac{111.7 \Omega}{111.7 + 120} = 4.339$$

$$V_{b2} = 9 \times \frac{135.1}{135.1 + 120} = 4.766 V, V_{b1} - V_a = 0 V, V_{b2} - V_a = 0.427 V$$

- Wheatstone bridge o/p Range (0 ~ 0.427 V)

- VFC o/p Range (0 ~ 3.8125 KHZ)


- Counter o/p " ($\frac{1}{180}$ sec) \Rightarrow (0 ~ 21.18 Pulse)

b) $T=55^\circ \rightarrow$ Counter o/p \Rightarrow !?

$$(55 \times 0.39) + 100 = 121.45 \Omega \Rightarrow V_b = 9 \times \frac{121.45}{121.45 + 120} = 4.527$$

$$V_b - V_a = 0.188 V \Rightarrow 0.188 \times \frac{10 KHZ}{1.12 V} = 1.678 KHZ$$
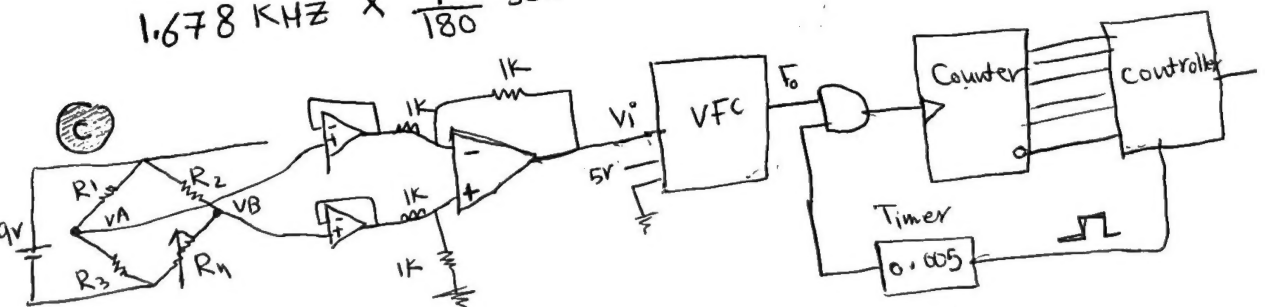
$$1.678 KHZ \times \frac{1}{180} \text{ sec} = 9.32 \text{ Pulse \#}$$



Q(3) 0.14 mA/g ($\pm 20\text{g}$) @ $0\text{g} = 5.2 \text{ mA}$
 $R = 190 \Omega$ (8 bit) ADC $\pm 4 \text{ V}$ reference

$$((-20 \times 0.14) + 5.2) \sim ((20 \times 0.14) + 5.2) \Rightarrow (2.4 \sim 8 \text{ mA}) \text{ sensor o/p}$$

$$(0.456 \text{ V} \sim 1.52 \text{ V}) \text{ Range in Volt}, (142 \sim 176) \text{ Digital o/p}$$

$$\Delta = \frac{8}{2^8} = 0.03125, \text{ Digital o/p} = \frac{\text{analog I/P} + 4}{\Delta V}$$

$$(1000110 \sim 10110000) \text{ o/p Range in binary}$$

△ Digital o/p for 8g

$$(8 \times 0.14) + 5.2 = 6.32 \text{ mA} \rightarrow 6.32 \times 190 = 1.2 \text{ V}$$

$$(1.2 + 4) / 0.03125 = 166 \rightarrow (10100110)_2$$

△ acceleration value if a/p (0D, 92)

$$\text{analog I/P} = -3.594 \text{ V}, 0.5625 \text{ V}$$

$$\text{in mA} = \text{out of Range}, 2.9 \text{ mA}$$

$$\text{acceleration} = , -16.42 \text{ g}$$

$$(00001101)_2, (10010010)_2$$

$$\Downarrow \quad \Downarrow$$

$$(13)_{10} \quad (146)_{10}$$

△ $F_s = 120 \text{ Hz}$, $F_N = 15 \text{ KHz}$, attenuate Noise 18%.

$$18\% = \frac{1}{\sqrt{1 + \left(\frac{15 \text{ KHz}}{F_c}\right)^2}} \Rightarrow F_c = 2745 \text{ Hz}$$

$$\text{effect on The o/p} = \frac{1}{\sqrt{1 + \left(\frac{120}{2745}\right)^2}} = 99.9\% \quad \text{very Good}$$

"Low Pass Filter"

Q(4)

$^{\circ}\text{C}$	0	5	10	15	20
R	103.6	105.1	106.3	107.1	108.3
	①		⑥		②

$$T_m = 12.4^{\circ}\text{C}$$

$$R(T) = R(T_0) (1 + \alpha \Delta T + \alpha_2 \Delta T^2)$$

$$108.3 = (106.3) (1 + 2.211 \times 10^{-3} (10) + \alpha_2 (10)^2)$$

$$\alpha_2 = -3.295 \times 10^{-5}$$

$$\alpha = \frac{1}{R(T_0)} \times \frac{R_2 - R_1}{T_2 - T_1}$$

$$= \frac{1}{106.3} \times \frac{108.3 - 103.6}{20 - 0}$$

$$= 2.211 \times 10^{-3}$$

$$T = 12.4^{\circ}\text{C} \rightarrow \Delta T = 2.4$$

$$R(T) = 106.3 (1 + 2.211 \times 10^{-3} \times 2.4 + 3.295 \times 10^{-5} \times (2.4)^2)$$

$$R(T) = 106.84 \Omega$$

Final Fall 2018

Q(1) RTD-PT100 ($22 \sim 190^{\circ}\text{C}$) \rightarrow ($0 \sim 3\text{V}$), ADC, Voltage Divider
 $V_s = 9\text{V}$, $R_1 = 200$

$$\triangle \left((22 \times 0.39) + 100 \right) \sim \left((190 \times 0.39) + 100 \right) \Rightarrow (108.58 \sim 174.1 \Omega)$$

$$V_1 = 9 \times \frac{108.58}{108.58 + 200} = 3.16, V_2 = 9 \times \frac{174.1}{174.1 + 200} = 4.18, (3.16 \sim 4.18 \text{ V})$$

$$0 = 3.16 \text{ M} + \text{offset}$$

$$3 = 4.18 \text{ M} + \text{offset}$$

$$3 = 1.02 \text{ M}$$

$$M = 2.94$$

$$\text{offset} = -9.29$$

$$[V_0 = 2.94 \text{ V} - 9.29]$$

$$\frac{102}{1018}$$

$$\Delta V = \frac{3}{2^8} = 0.0117$$


$$\text{Digital o/p} = \frac{\text{analog I/P}}{0.0117}$$

$$(255)_{10}$$

$$(4096)_{16}$$

$$(0 \sim 256)_{10}$$

3

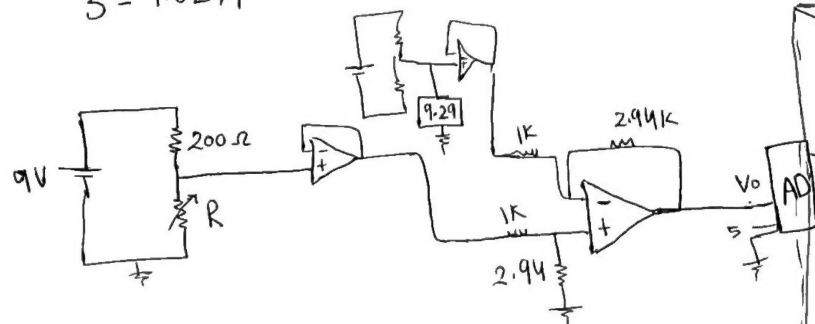

C 100°C

$$(100 \times 0.39) + 100 = 139 \text{ g} \Rightarrow 9 \times \frac{139}{139 + 200} = 3.69 \text{ v}$$

$$V_o = 2.94 \times 3.69 - 9.29 = 1.5586 \text{ V} \# \quad , \text{ Digital O/P} = 133$$

فی حاجۃ منی مفہومہ فی "ع" ۱۹! لکن الاقامہ کا

Q2) $S = 0.14 \text{ mA/g}$, $@ \theta_g = 7 \text{ mA}$ ($\pm 30^\circ$), VFC (4V/6kHz)

⑧ $(-30 \times 0.14) + 7 = 2.8 \text{ mA}, (30 \times 0.14) + 7 = 11.2 \text{ mA}, (2.8 \sim 11.2 \text{ mA})$


$$R = 100\Omega \rightarrow (0,28\text{ V} \sim 1,2\text{ V})$$

$$\frac{1}{4/6} \frac{\text{kHz}}{\text{V}} \rightarrow (0.42 \text{ kHz} \sim 1.68 \text{ kHz})$$

$T = 0.2 \text{ sec} \rightarrow (84 \sim 336 \text{ Pulse}) \rightarrow (01010100, 10101000)_2$

③ $(-0.5g) \rightarrow (-0.5 \times 0.14) + 7 = 6.93 \text{ mA} \times 100 \text{ } \Omega = 0.693 \text{ V}$
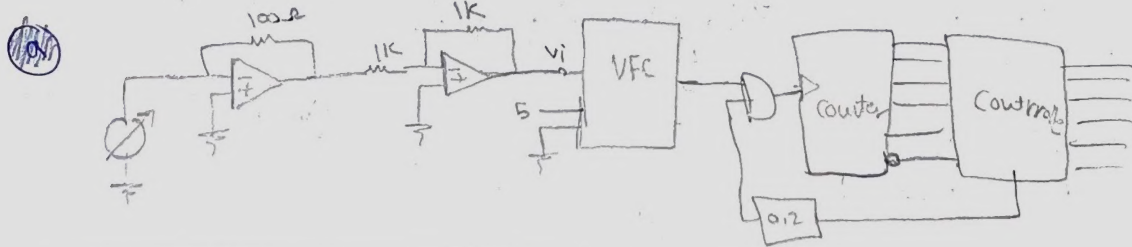
$$\rightarrow 1.0395 \text{ KHz} \times 0.2 \text{ sec} = 208 \text{ Pulse} \rightarrow (1106000)_2$$




$Q_{(3)} \quad S = 5 \text{ mV/bar} \quad , \quad 5 \Omega/\text{cm} \quad \text{PoT} \quad , \quad 150 \text{ cm}$

$(V_s = 9V, R_1 = 150\Omega)$ Green $L > 70\mu m$
 $P < 5bar$

ref ✓ mio olog d
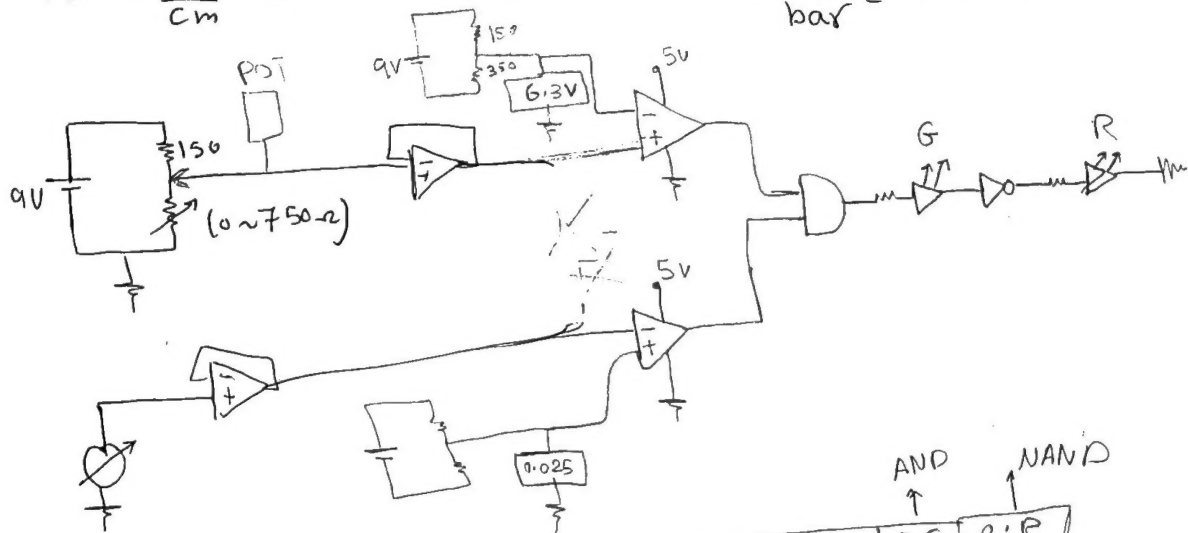
$$150 \times \frac{5\Omega}{\text{cm}} = 750\Omega, \quad 5\text{bar} \times \frac{5\text{mV}}{\text{bar}} = 25\text{mV}$$



A	B	AND	NAND
		O.F	O.R
0	0	0	X
0	1	0	1
1	0	0	1
1	1	1	0

Q(4) $\bar{A} \cdot B \cdot C$

Q(5) $V = 19\text{mV}$ $T = ?$, $T = -40^\circ$ $V = ?$ K-Type
 $V = -1.50\text{mV}$

$$V_L = 18.94, \quad V_H = 19.15$$

$$T_L = 460, \quad T_M = 465$$

$$V_m = V_L + \left(\frac{T_M - V_L}{T_M - T_L} \right) (T_m - T_L) \Rightarrow 19 = 18.94 + \left(\frac{19.15 - 18.94}{5} \right) (T_m - 460)$$

$$T_m = 461.43^\circ$$

Final Spring 2018

Q(2) $S = 5\text{mV}/^\circ\text{C}$, $(30 \sim 120^\circ\text{C})$, VFC $(2\text{V}/\text{KHz})$

sensor o/p Range $(30 \times 5 \sim 120 \times 5) \rightarrow (0.15 \sim 0.6\text{V})$

VFC o/p Range $(0.15 \times \frac{1}{2/1} \sim 0.6 \times \frac{1}{2}) \rightarrow (75 \sim 300\text{Hz})$

count o/p Range $(75 \times \frac{1}{10} \sim 300 \times \frac{1}{10}) \rightarrow (7.5 \sim 30\text{ pulse})$

$$T = 112^{\circ}\text{C} \rightarrow 112 \times 5 \frac{\text{mV}}{^{\circ}\text{C}} = 0.56 \text{ V} \rightarrow 0.56 \text{ V} \times 0.5 \frac{\text{kHz}}{\text{V}} = 0.28 \text{ kHz}$$

$$280 \text{ Hz} \times \frac{1}{10} = 28 \text{ Sample } \#$$

$$Q(3) \quad S = 0.13 \text{ mA / bar} \quad , \quad (-20 \sim +20 \text{ g}) \quad , \quad @ \quad \theta_{\text{bar}} = 4 \text{ mA} \quad , \quad R = 150 \Omega$$

ADC (8bit, $\pm 4\text{V}$ ref)

$$\text{Sensor o/p} \quad (-20 \times 0.13) + 4 \sim (20 \times 0.13) + 4 \Rightarrow (1.4 \sim 6.6 \text{ mA})$$

$$\Rightarrow (1.4 \times 150 \sim 6.6 \times 150) \Rightarrow (0.21 \sim 0.99 \text{ V}) \xrightarrow{\text{Digital o/p} \rightarrow} (135 \sim 160)$$

$$\Delta V = \frac{8}{2^8} = 0.03125 \quad \text{Digital o/p} = \frac{\text{analog I/P}}{0.03125}$$

$$\Delta (P = 8 \text{ bar}) \Rightarrow (8 \times 0.13) + 4 = 5.04 \text{ mA} \times 150 \Omega = 0.756 \text{ V}$$

$$\text{Digital o/p} = \frac{0.756 + 4}{0.03125} = \left(\frac{152}{10} \right) \rightarrow \left(\begin{matrix} 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \\ 1 & 0 & 0 & 1 & 1 & 0 & 0 & 0 \end{matrix} \right)_2$$

$$\Delta (\text{Digital o/p} = 18H) \Rightarrow (18)_H = (00011000)_2 = (24)_{10}$$

$$\text{analog I/O} = (24 \times 0.03125) - 4 = -3.25 \text{ V OUT OF RANGE}$$

Q(4) "رقة في الورقة"

$$DAC = \left(\begin{matrix} 0 & 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 0 & 1 & 0 & 1 & 0 & 1 & 0 & 1 \end{matrix} \right)_2 \Rightarrow (85)_{10} \Rightarrow \text{analog I/P} (0.664)_{\text{volt}}$$

$$\Delta V = \frac{2}{2^8} = 7.8125 \times 10^{-3} \quad , \quad \text{Digital o/p} = \frac{\text{analog I/P}}{7.8125 \times 10^{-3}}$$

$$V_o = \left(\frac{R_f}{R} + 1 \right) V_i = \left(\frac{1.7}{1} + 1 \right) \times 0.664 = 1.7928 \text{ V } \#$$

$$\Delta V = \frac{5}{2^8} = 0.0195 \quad , \quad \text{Digital o/p} = \frac{1.7928}{0.0195} = (92)_{10}$$

$$(0101100)_{2}$$

(5) $R_{ref} = 40^\circ C$

$V = ?$ if $T = 120^\circ C$

J-Type

△

$$V_{J40}(120) = V_{J0}(120) - V_{J0}(40)$$

$$6.36 - 2.06 = 4.3 \text{ mV}$$

△

	①		②		③
C°	0	5	10	15	20
R	107.6	109.1	110.2	111.7	113.7

$$T = 11.4^\circ C$$

$$R(T) = R(T_0) * (1 + \alpha_1 \Delta T + \alpha_2 \Delta T^2) \quad , \quad \alpha = \frac{1}{R(T_0)} \cdot \frac{R_2 - R_1}{T_2 - T_1}$$

Assume $R(T) = 111.7$

$$111.7 = 110.2 \times (1 + 1.86 \times 10^{-3} \times 10 + \alpha_2 \times 100)$$

$$\alpha = \frac{1}{110.2} \cdot \frac{111.7 - 107.6}{20}$$

$$\alpha_2 = -4.98 \times 10^{-5}$$

$$\alpha = 1.86 \times 10^{-3} \text{ } \#$$

$$T = 11.4^\circ C \rightarrow$$

$$R(T) = 110.2 \times (1 + 1.86 \times 10^{-3} \times (11.4 - 10) - 4.98 \times 10^{-5} \times (11.4 - 10)^2)$$

$$R(T) = 110.47^\circ C \text{ } \#$$

Final Spring 2017

Q11) $S = 4 \Omega / ^\circ C$ ($\pm 25^\circ C$) @ $0^\circ C = 280 \Omega$, Wheatstone $\frac{V}{V}$ + use Transm

(8bit, 0~5V) ADC

$$((-25 \times 4) + 280 \sim (25 \times 4) + 280) \rightsquigarrow (180 \Omega \sim 380 \Omega)$$

$$R_1 = 100, R_2 = 120, V_s = 9V$$

$$R_1 R_4 = R_2 R_3$$

$$100 \times 180 = 120 \times R_3 \rightarrow R_3 = 150 \Omega$$

$$V_a = 9 \times \frac{150}{150 + 100} = 5.4V, V_{b1} = 9 \times \frac{180}{180 + 120} = 5.4V$$

$$V_{b2} = 9 \times \frac{380}{380 + 120} = 6.84V \rightsquigarrow (0 \sim 1.44 \text{ Volt})$$

$$V_o = V_i + 1 \text{ using Transm} \rightsquigarrow (1 \sim 2.44 \text{ Volt})$$

7

$$\Delta V = \frac{5}{2^8} = 0.0195$$

$$(51 \sim 125)_{10} \rightarrow \text{Digital O/P}$$

$$(00110011, 0111101)_2$$

$$\Delta T = -2^\circ\text{C} \rightarrow (-2 \times 4) + 280 = 272 \text{ }^\circ\text{C}$$

$$V_b = 9 \times \frac{272}{272 + 120} = 6.24 \rightarrow (6.24 - 5.4) = 0.844 \text{ V} + 1 = 1.844$$

$$\text{Digital O/P} = (94)_{10} \rightarrow (01011110)_2$$

$$Q(2) \quad S = 0.33 \text{ mA/g} \quad (\pm 20g) \quad \text{ADC (8bit, } \pm 4)$$

$$\text{Sensor O/P } (-20 \times 0.33) \sim (20 \times 0.33) \Rightarrow (-6.6 \sim 6.6 \text{ mA}) \quad \text{Assume } R = 100\Omega$$

$$(-0.66 \sim 0.66 \text{ V}) \quad \left[\text{need Transmitter } (0.34 \sim 1.66 \text{ V}) \right] \rightarrow \text{محول}$$

$$\Delta V = \frac{8}{2^8} = 0.03125, \quad (107 \sim 149)_{10} \rightarrow \text{Digital O/P}$$

$$\Delta (-3g) \rightarrow -3 \times 0.33 = -0.99 \text{ mA} \times 100 = -0.099 \text{ V}$$

$$\text{Digital O/P} \rightarrow (124)_{10} \rightarrow (01111100)_2$$

$$\Delta (06H) \rightarrow (00000110)_2 \rightarrow (6)_{10} \quad \text{OUT OF RANGE}$$

$$Q(3) \quad (10 \text{ bit } 10 \sim 5 \text{ V}) \text{ ADC, Sensor O/P } (\pm 150 \text{ mV})$$

$$F_s = 15 \text{ Hz}, \quad V_N = 20 \text{ mV}, \quad f_N = 150 \text{ Hz}, \quad \text{attenuate } (25\%)$$


$$\Delta V = \frac{5}{2^{10}} = 4.88 \times 10^{-3}$$

$$25\% = \frac{1}{\sqrt{1 + \left(\frac{150}{F_c}\right)^2}} \Rightarrow F_c = 38.72 \text{ Hz}$$

$$V_o/V_i = \frac{1}{\sqrt{1 + \left(\frac{15}{38.72}\right)^2}} = 0.9324 \sim 93.2\% \quad \text{Good}$$

$$\Delta V_0 (-150 \text{ mV} \sim 150 \text{ mV}) \xrightarrow{+20 \text{ mV}} (-0.13 \sim 0.17 \text{ V})$$

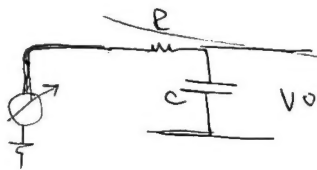effect of filter in sensor o/p $(-0.13 \times 0.9324) \sim (0.17 \times 0.9324)$
 $(-0.12 \sim 0.16 \text{ V}) \#$



$$V_o = V_i + 1 \rightarrow (0.88 \sim 1.16 \text{ V})$$

Digital o/p $(180 \sim 237)_{10}$

$$(00010100, 0011101101)_2$$

Q(u) Type-J

$$\Delta T = 32^\circ\text{C} \quad V = ?$$

$$\Delta T > 32^\circ\text{C} \rightarrow \text{ON Cooler}$$


$$\Delta T_L = 30, V_L = 1.54$$

$$T_H = 35, V_H = 1.8$$

$$T_m = T_L + \left(\frac{T_H - T_L}{V_H - V_L} \right) (V_m - V_L)$$

$$32 = 30 + \left(\frac{5}{0.26} \right) (V_m - 1.54)$$

$$V_m = 1.644 \#$$

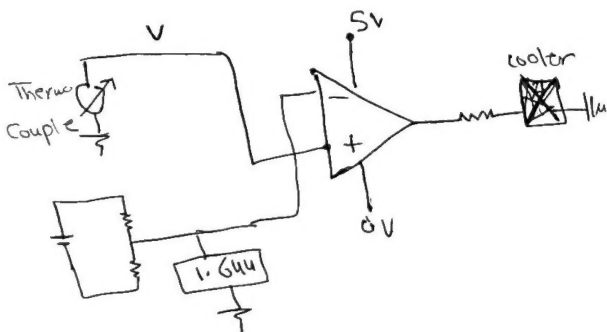

$$\Delta T = 13^\circ\text{C} \rightarrow R = ?$$

$$T < 13 \rightarrow \text{ON heater}$$

	1	0	2		
$^{\circ}\text{C}$	0	5	10	15	20
Ω	107.6	109.1	110.2	111.3	111.7

$$\alpha = \frac{1}{R(T_0)} \times \frac{R_2 - R_1}{T_2 - T_1} = 1.86 \times 10^{-3}$$


$$R(T) = R(T_0) (\alpha \Delta T + 1)$$

$$R(T) = 110.2 (1 + 1.86 \times 10^{-3} \times 3)$$

$$R(T) = 110.8 \Omega \#$$

$$V = 9 \times \frac{110.8}{110.8 + 120} = 4.32 \text{ V} \#$$

Assume $R = 120\Omega$, $V_s = 9V$

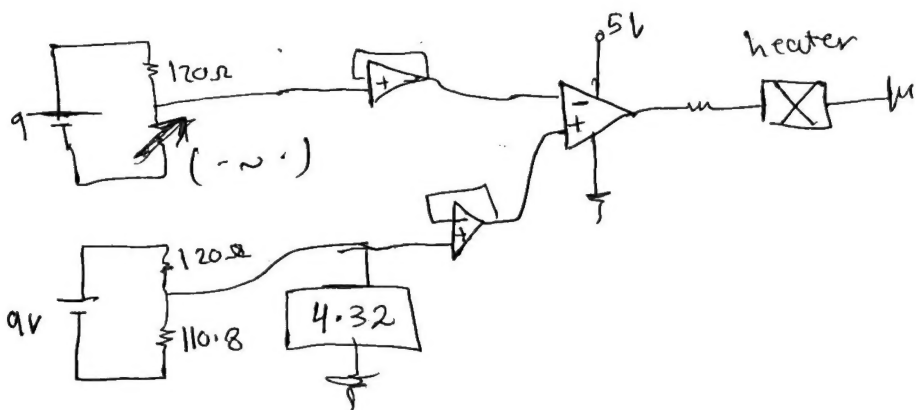

Q(13) S-19 Final

$$\Delta (0.456 \text{ V} \sim 1.52 \text{ V})$$

$$-4 = 0.456M + F$$

$$4 = 1.52M + F$$

$$8 = 1.064M$$

$$M = 7.518$$

$$F = -7.428$$

$$V_o = 7.518 \text{ V}; -7.428$$

$$\left[\begin{matrix} (-4 \sim 4 \text{ V}) \\ (0 \sim 256)_{10} \end{matrix} \right]_{10}$$

$$\Delta (89 \times 0.14) + 5.2 = 6.32 \text{ mA} \times 190 \Omega = 1.2 \text{ V} \rightarrow 1.5936 \text{ V}$$

$$\text{Digital o/p} \approx (\cancel{178})_{10} \rightarrow (1011000)_2$$

$$\Delta \text{ oD} \rightarrow 13, 92 \rightarrow 146$$

$$D_o \times \Delta V = -3.59, 0.5625$$

$$V_o = V_i M + F = 0.51 \text{ V},$$

$$1.6628 \text{ V}$$

$$V/R = I = 2.68 \text{ mA},$$

$$5.59 \text{ mA}$$

$$g = -18 \text{ g},$$

$$2.79 \text{ g}$$

Q(13) S-18 Final

$$(0.21 \sim 0.99) \text{ V},$$

$$-4 = 0.21M + F$$

$$4 = 0.99M + F$$

$$8 = 0.78M$$

$$M = 10.25$$

$$F = -6.65$$

$$V_o = 10.25 \text{ V}; -6.65$$

$$\Delta (8 \times 0.13) + 4 = 5.04 \text{ mA} \times 150 \Omega = 0.756 \text{ V} \rightarrow \cancel{2.2} \text{ V} \rightarrow 1.599$$

$$(179)_{10} \rightarrow (10110011)_2$$

$$\Delta (18)_H \rightarrow (24)_{10}$$

$$\rightarrow -3.25 \text{ V} \rightarrow 0.28 \text{ V} \rightarrow 1.88 \text{ mA}$$

$$(-16.25)_9$$